

# SIMULATION AND IMPLEMENTATION OF LOGIC GATES , ADDERS AND SUBTRACTORS

## AIM:

To simulate the following logic circuits using Vivado 2023.2.

- 1) Logic Gates
- 2) Adders
- 3) Subtractors

## APPARATUS REQUIRED:

VIVADO 2023.2

## PROCEDURE:

STEP:1 Launch the Vivado 2023.2 software.

STEP:2 Click on “create project ” from the starting page of vivado .

STEP:3 Choose the design entry method:RTL(verilog/VHDL)

STEP:4 Crete design source and give name to it and click finish.


STEP:5 Write the verilog code and check the syntax.

STEP:6 Click “run simulation” in the navigator window and click “Run behavioral simulation”.

STEP:7 Verify the output in the simulation window.

## LOGIC GATES

## LOGIC DIAGRAM

 

## VERILOG CODE

```

module logicgate(a,b,andgate,orgate,nandgate,norgate,xorgate,xnorgate,notgate);
input a,b;
output andgate,orgate,nandgate,norgate,xorgate,xnorgate,notgate;

and(andgate,a,b);

or(orgate,a,b);

nand(nandgate,a,b);

nor(norgate,a,b);

xor(xorgate,a,b);


xnor(xnorgate,a,b);

not(notgate,a);

Endmodule


```

## OUTPUT WAVEFORM

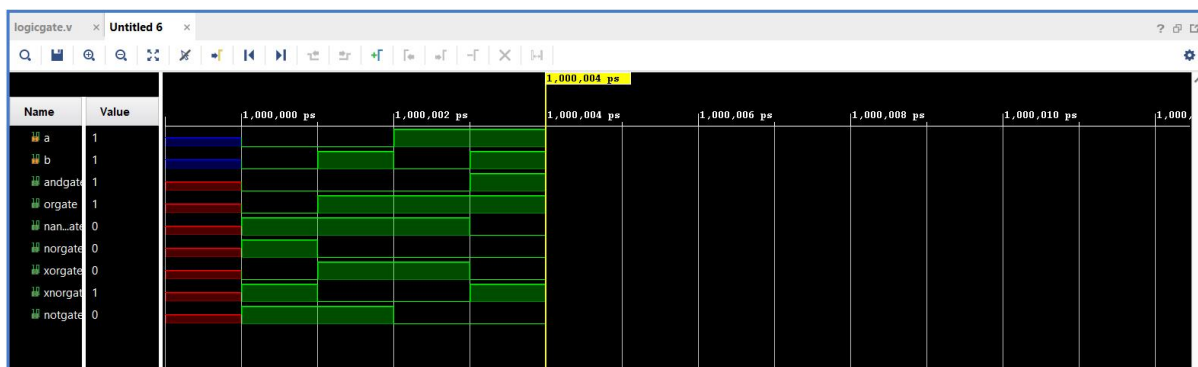

## HALF ADDER

### LOGIC DIAGRAM

 

Truth Table			
Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


## VERILOG CODE

```

module half_adder(a,b,sum,carry);
input a,b;
output sum,carry;
xor g1(sum,a,b);
and g2(carry,a,b);
endmodule


```

## OUTPUT WAVEFORM

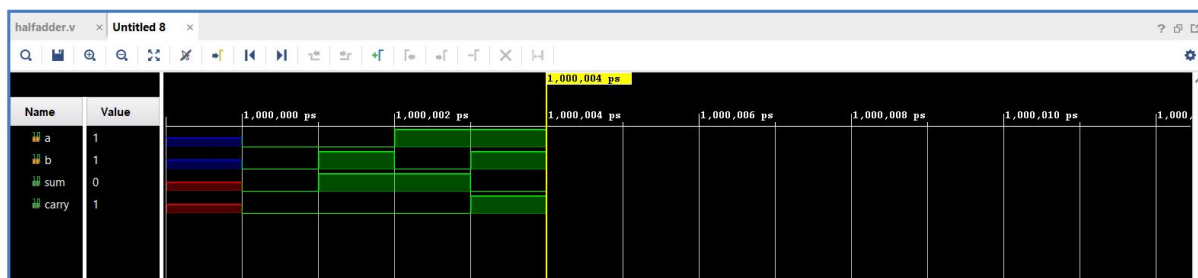

## FULL ADDER

### LOGIC DIAGRAM

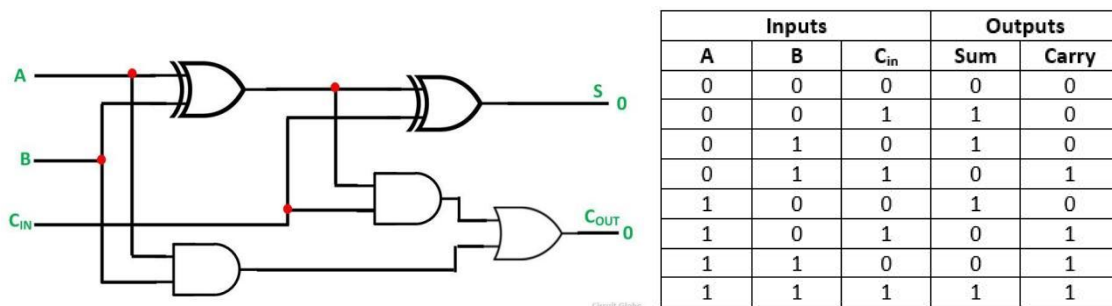

## VERILOG CODE

```

module fulladder(a,b,c,sum,carry);
input a,b,c;
output sum,carry;
wire w1,w2,w3;
xor(w1,a,b);
xor(sum,w1,c);
and(w2,w1,c);
and(w3,a,b);

```

```
or(carry,w2,w3);
```


```
endmodule
```

## OUTPUT WAVEFORM



## HALF SUBTRACTOR

### LOGIC DIAGRAM

 

Inputs		Outputs	
A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

## VERILOG CODE

```
module halfsub(a,b,diff,borrow);
```

```
input a,b;
```


```
output diff,borrow;
```

```
xor(diff,a,b);
```

```
and(borrow,~a,b);
```


```
endmodule
```

## OUTPUT WAVEFORM

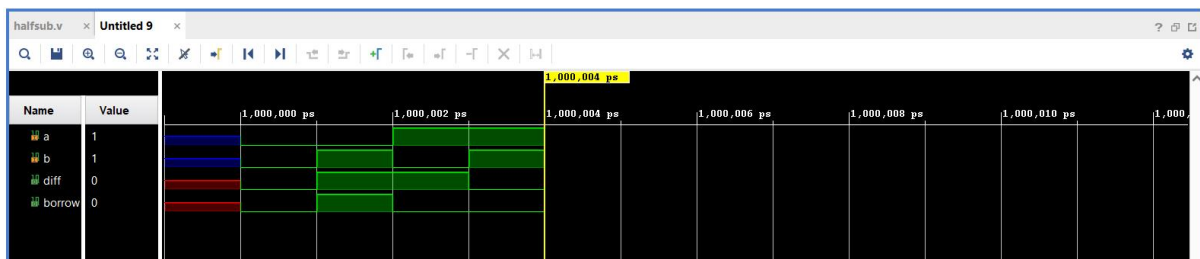

## FULL SUBTRACTOR

### LOGIC DIAGRAM

 

Inputs			Outputs	
A	B	Borrow <sub>in</sub>	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

### VERILOG CODE

```
module fs(a,b,bin,d,bout);
```

```
input a,b,bin;
```

```
output d,bout;
```

```
wire w1,w2,w3;
```

```
xor(w1,a,b);
```

```
xor(d,w1,bin);
```


```
and(w2,~a,b);
```

```
and(w3,~w1,bin);
```

```
or(bout,w3,w2);
```


```
endmodule
```

### OUTPUT WAVEFORM

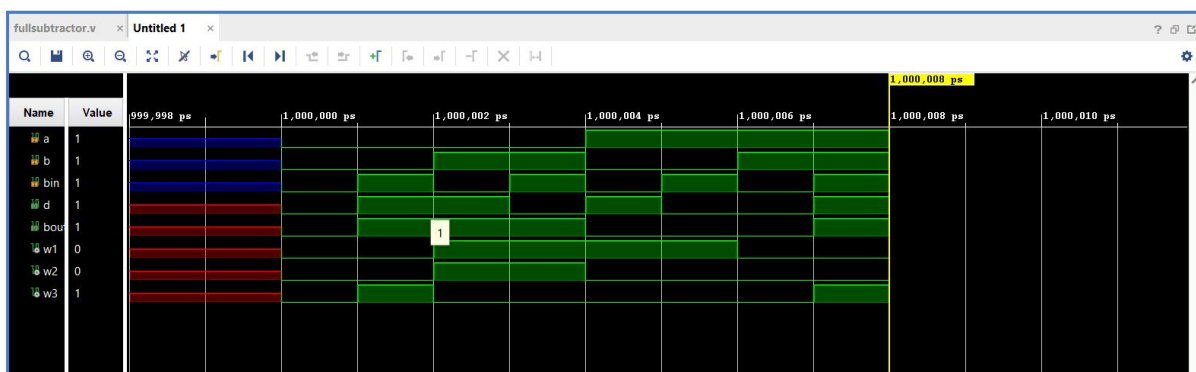

## RIPPLE CARRY ADDER

### LOGIC DIAGRAM

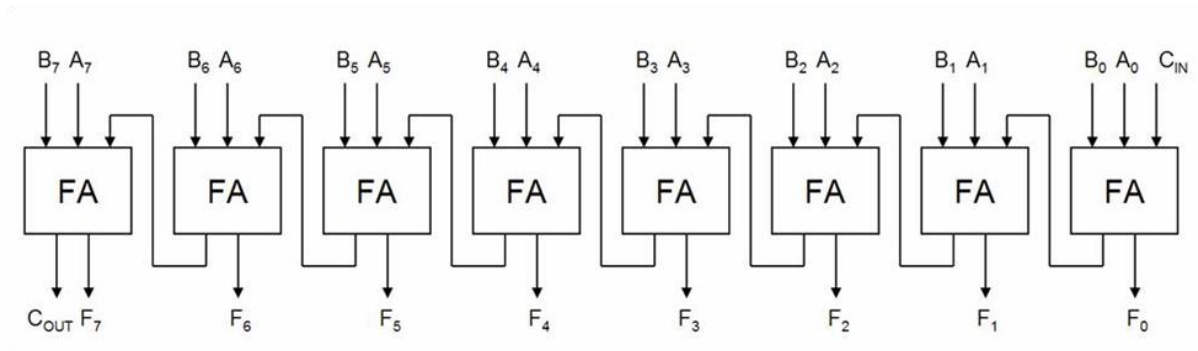

### VERILOG CODE

```
module fulladder(a,b,c,sum,carry);
```

```
input a,b,c;
```

```
output sum,carry;
```

```
wire w1,w2,w3;
```

```
xor(w1,a,b);
```

```
xor(sum,w1,c);
```

```
and(w2,w1,c);
```

```
and(w3,a,b);
```

```
or(carry,w2,w3);
```

```
endmodule
```

```
module rca_8bit(a,b,cin,s,cout);
```

```
input [7:0]a,b;
```

```
input cin;
```

```
output [7:0]s;
```

```
output cout;
```

```
wire [7:1]w;
```

```
fulladder f1(a[0], b[0], cin, s[0], w[1]);
```

```
fulladder f2(a[1], b[1], w[1], s[1], w[2]);
```

```
fulladder f3(a[2], b[2], w[2], s[2], w[3]);
```

```
fulladder f4(a[3], b[3], w[3], s[3], w[4]);
```


```
fulladder f5(a[4], b[4], w[4], s[4], w[5]);
```

```

fulladder f6(a[5], b[5], w[5], s[5], w[6]);
fulladder f7(a[6], b[6], w[6], s[6], w[7]);
fulladder f8(a[7], b[7], w[7], s[7], cout);
endmodule

```

## OUTPUT WAVEFORM

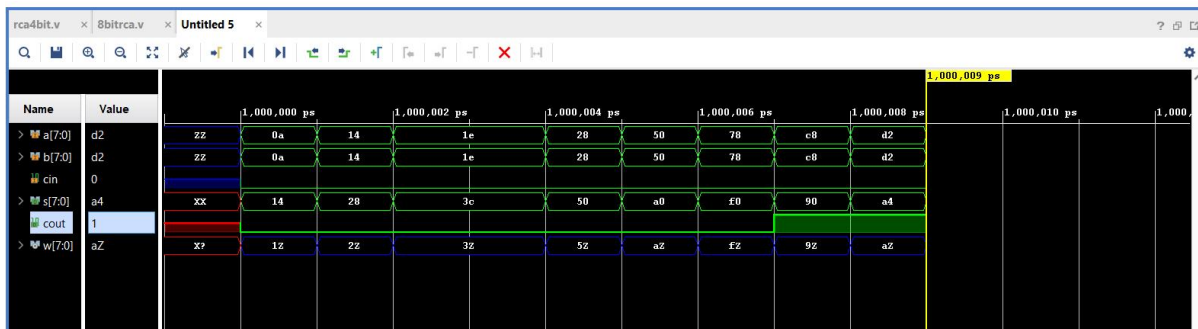

## RESULT:

Thus the simulation and implementation of logic gates, adders and subtractors has done and outputs are verified successfully.